

# Ohm's Law


It's just 9 new eq<sup>n</sup>. How hard can it be?

1st let's review some Jr. Science (grade 9):

▶ Electric Current: Cras...

More review (if you need it):

▶ Electric Circuits: Basi...

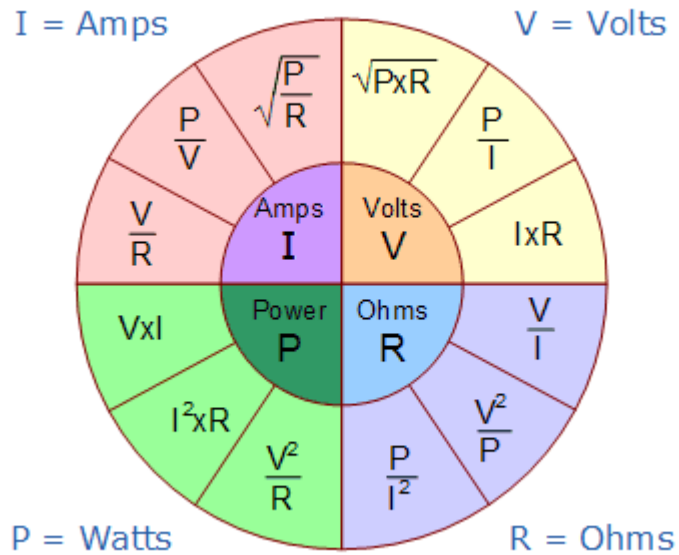

Ohm's Law:

$$V = IR$$

V = Volts, I = Current, R = Resistance

**Current: This is the number of charged particles flowing through a circuit per second**

The charge of a particle is measured in Coulombs (a single electron / proton / positron / antiproton has a charge of:  $1.6 \times 10^{-19}$  C.

One Coulomb is extremely tiny!

Q = It where:

$$Q = It$$

Q is total charge of particles  
I is current (in Amperes, A)

t is time (in seconds)

Eg: If 4 amps of current flows for 5 seconds, how many electrons flow?

$$Q = 4(5) = 20$$
$$20 \cdot \frac{1}{1.6 \times 10^{-19} \text{ C}} = 1.25 \times 10^{20} \text{ electrons.}$$

**Voltage:** This is the change in electric potential per charge

As electrons flow through the circuit they gain potential energy as they flow through a battery and lose potential energy as they flow through devices in the circuit.

This is the driving force behind current flow.

**Resistance:** This is a measure of the opposition to current flow in a circuit

It is measured in the units of Ohms  $\Omega$  This is the Greek letter 'Omega'.

We control the resistance of a circuit by adding / subtracting devices or pathways.

Enough definitions.

"Let's get this party started"

--J. Bieber, 2009

A lightbulb has a resistance of  $20 \Omega$ . If  $0.6 \text{ A}$  is flowing through it, what is the voltage drop across the light bulb?

Hint: 12 V

$$R = 20 \Omega$$
$$I = 0.6 \text{ A}$$
$$V = ?$$

$$V = \frac{3(20)}{5} = 12 \text{ V}$$



3 A flows through a lightbulb with a voltage drop of 6 V, what is the resistance?

Hint: 2 Ω

$$\begin{aligned}
 I &= 3 & V &= IR \\
 V &= 6 & 6 &= 3R \\
 R &=? & \frac{6}{3} &= R \\
 & & 2\Omega &= R
 \end{aligned}$$

Power: In an electrical circuit this is the rate at which electrical energy is transformed in a device

$$P = IV$$



P is power, in Watts (W), I is current (A), V is voltage, (V)

This eq<sup>n</sup> can be combined with Ohm's Law to give 9 eq<sup>n</sup>!  
It's equation-ception!

$$P = IV$$

$$\begin{aligned}
 V &= IR \\
 \frac{V}{R} &= I
 \end{aligned}$$

See top circle of eq<sup>n</sup>.

$$P = I(IR)$$

$$P = I^2R$$

$$P = \frac{V}{R} V$$

$$\begin{aligned}
 \frac{P}{V} &= I & V &= IR \\
 & & & \frac{V}{V}
 \end{aligned}$$

$$P = \frac{V^2}{R}$$

YO DAWG, I HEARD YOU LIKE EQUATIONS,

SO I PUT AN EQUATION IN YOUR EQUATION  
SO YOU COULD EQUATION WHILE YOU EQUATION.

imgflip.com

The current through a resistor is 4 A.  
If the voltage drop is 12 V, what is the  
power of the resistor?

$$I = 4 \quad V = 12 \quad P = ? \quad \text{Hint: 48 W}$$

$$\begin{aligned} P &= IV \\ &= 4(12) \\ &= 48 \text{ W} \end{aligned}$$

A 60 W light bulb is placed in a circuit  
with a voltage drop of 120 V. What is  
the resistance of the bulb?

$$P = 60 \quad V = 120 \quad R = ? \quad \text{Hint: } 240 \text{ } \Omega$$

$$\begin{array}{l|l} P = IV & V = IR \\ 60 = I(120) & 120 = \frac{1}{2} R \\ \frac{60}{120} = I & 240 \text{ } \Omega = R \\ \frac{1}{2} = I & \end{array}$$