

Kirchoff's Laws

What Goes In,
Must Come Out



Rule 1: Current Rule

For any junction in a circuit the total current flowing into the junction must equal the total current flowing out of the junction

For any point in a circuit:

$$\Sigma I = 0$$

$$\Sigma_{in} = \Sigma_{out}$$

Power Source




Battery

$$V = IR$$



resistor

$$P = I(V)$$

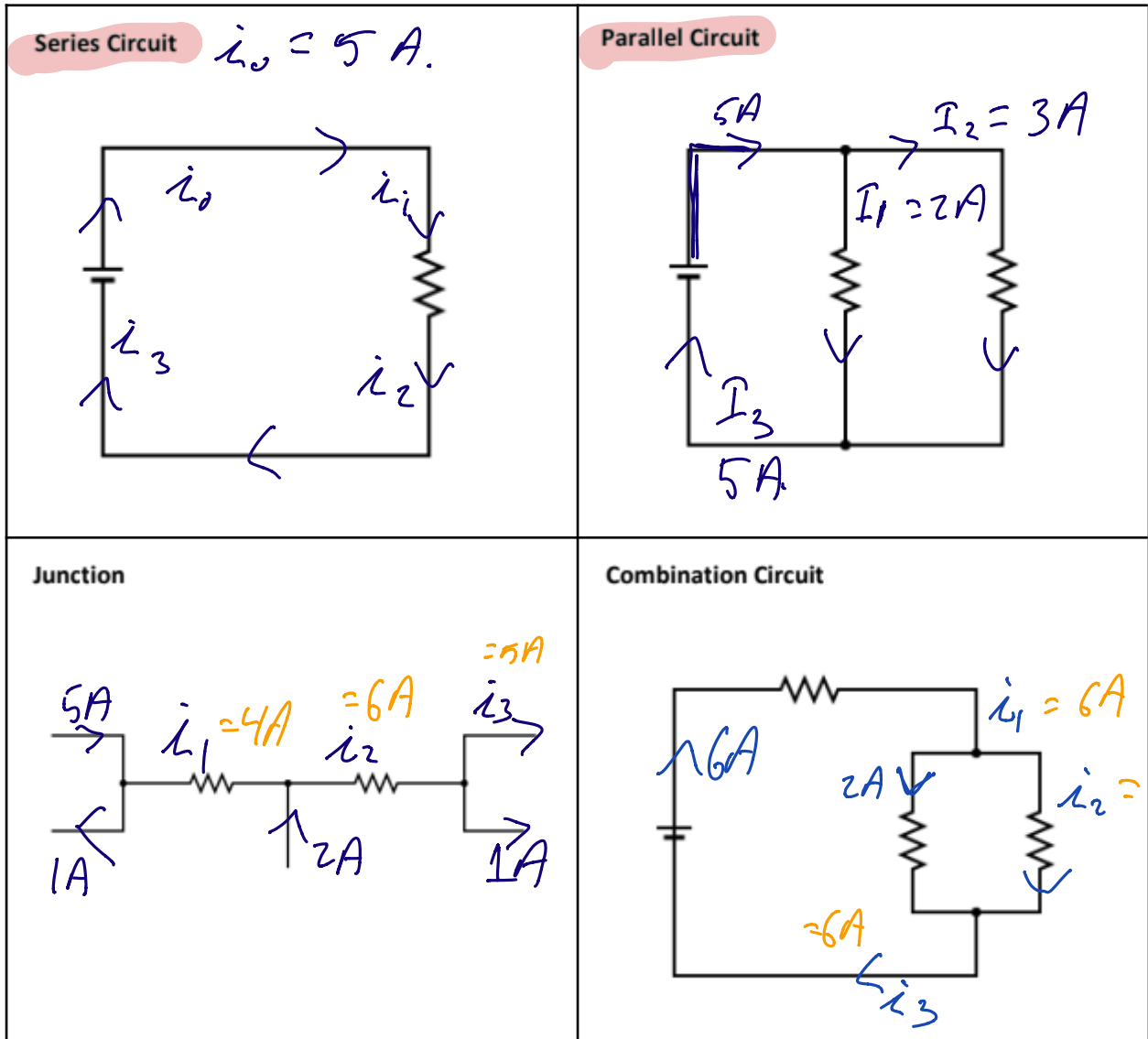

Rule 2: Voltage Rule

In any closed loop within a circuit the sum of all the voltages equals zero.

The total voltage gained equals the total voltage dropped

This is an example of conservation of energy

$$\Sigma V_{\text{gained}} = \Sigma V_{\text{dropped}}$$

Series Circuit

