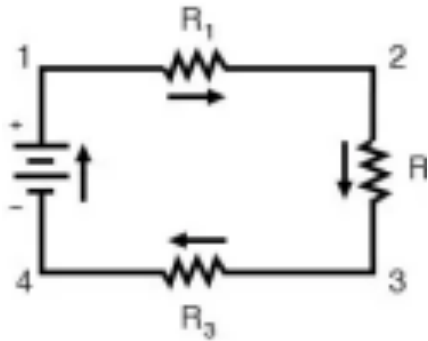


Series

In a series circuit there is only one path for the current to flow.

The current is the same everywhere in the path.



$$I_0 = I_1 = I_2 = I_3$$

The total resistance of the circuit is the sum of all the resistances.

$$R_T = R_1 + R_2 + R_3$$

The total voltage drop equals the voltage supplied by the power source.

$$V_T = V_1 + V_2 + V_3$$


Determine I if the power supply is set to 6 V and the resistance is

$$\boxed{V = IR}$$
$$P = IV$$

$$6 = I \cdot 12$$

$$\frac{6}{12} = I$$



$$0.5 \text{ A} = I$$

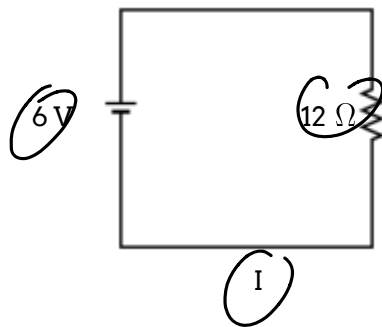

Determine I , V_1 and V_2 if the power supply is set to 24 V and ~~5 Ω~~

$$V_1 = IR = 3(5) = 15 \text{ V}$$

$$V_2 = IR = 3(3) = 9 \text{ V}$$

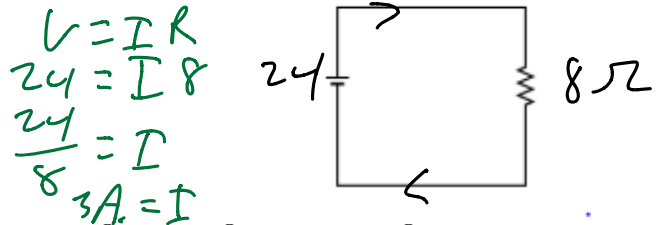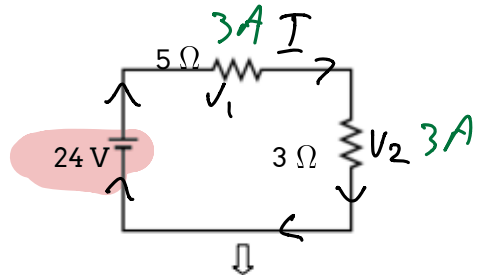


$$V = IR$$

$$24 = I(8)$$

$$\frac{24}{8} = I$$

$$3 \text{ A} = I$$

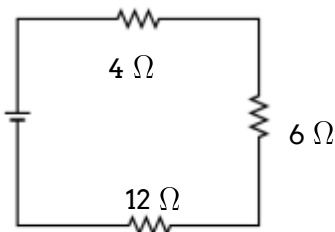
Determine the total voltage if the current is 2 A and R_1 is 4 Ω , R_2 is 6 Ω and R_3 is 12 Ω .



$$V = IR$$

$$= 2(22)$$

$$= 44 \text{ V}$$

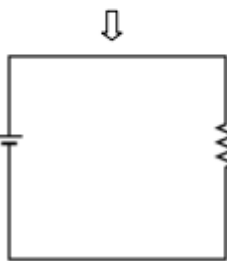


$$R_T = 4 + 6 + 12$$

$$= 10 + 12$$

$$= 10 + 10 + 2$$

$$= 20 + 2$$

$$= 22 \Omega$$

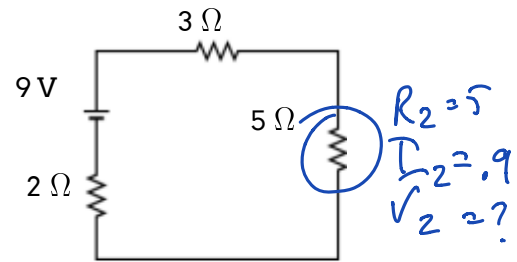

Determine the Power in R_2 .
 $R_1 = 3 \Omega$, $R_2 = 5 \Omega$, $R_3 = 2 \Omega$, Battery = 9 V

$$P = IV$$

$$V = IR$$

$$9 = I(10)$$

$$\frac{9}{10} = I$$

$$P = 0.9(9) = 8.1 \text{ W}$$

$$0.9 \text{ A} = I$$

P in R_T

$$V = IR$$

$$= 0.9(5)$$

$$V_2 = 4.5$$

$$P = IV$$

$$= 0.9(4.5)$$

$$= 4.05 \text{ W}$$

