
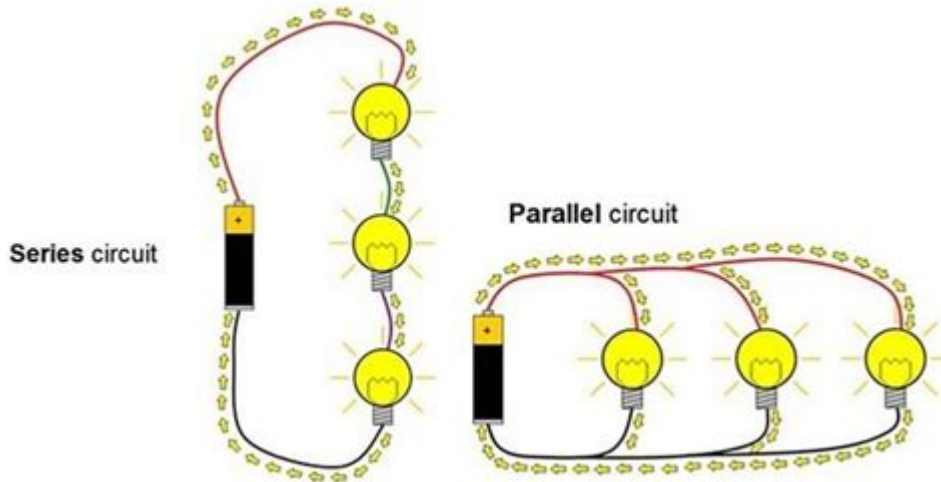


Parallel

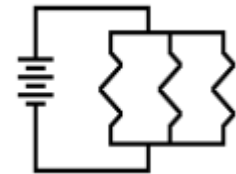

→ A parallel circuit has 2 or more pathways for the current to flow

→ The current through each pathway depends on the resistance of that pathway (the greater the resistance, the lower the current)



→ The sum of the current in the branches is equal to the current flowing into the junction.

$$\blacklozenge I_0 = I_1 + I_2 + I_3$$

→ The same voltage drop across parallel branches is the same in each branch

$$\blacklozenge V_1 = V_2 = V_3$$

→ The total resistance of a parallel section is calculated by:

$$\blacklozenge \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

• *solve for R_p

$$\frac{1}{R_p} = \frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R_1 R_2 R_3}$$



$$1 = \frac{R_p (R_2 R_3 + R_1 R_3 + R_1 R_2)}{R_1 R_2 R_3}$$

$$\frac{R_1 R_2 R_3}{R_2 R_3 + R_1 R_3 + R_1 R_2} = R_p$$

Determine I_0 , V_1 , V_2 , I_1 , and I_2 .
 Battery = 12 V, $R_{1,2} = 3 \Omega$,

- 1) Solve via Voltage loop
- 2) Solve via Thevenin Equivalence

1) $V = IR$
 $12 = I(3)$
 $4 = I$

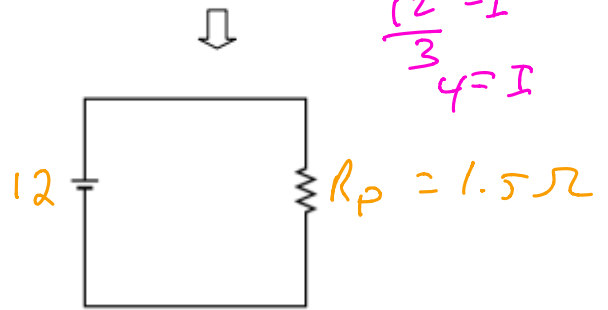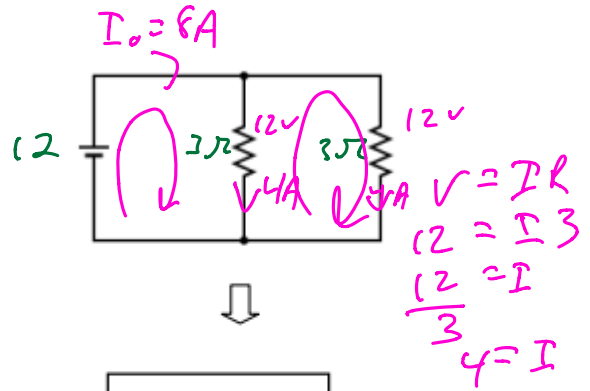


$V = IR$
 $12 = I \cdot 1.5$
 $\frac{12}{1.5} = I$
 $8A = I$

$I = \frac{2R_p}{3}$
 $3 = 2R_p$
 $\frac{3}{2} = R_p$


$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$
 $= \frac{1}{3} + \frac{1}{3}$

$\frac{1}{R_p} = \frac{2}{3}$

$R_p = \frac{3}{2} = 1.5 \Omega$

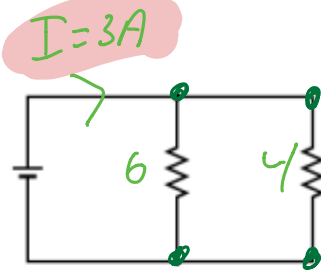

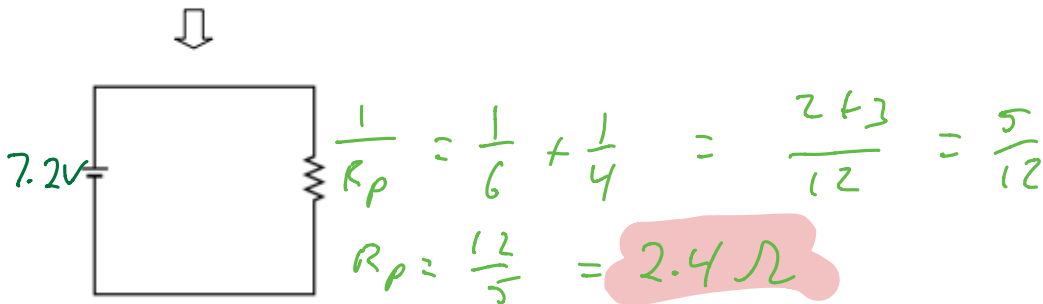Determine V_{Total} , $I_{1,2}$
 $I_0 = 3A$, $R_1 = 6 \Omega$, $R_2 = 4 \Omega$



$V = IR$
 $V = 3(2.4)$
 $= 7.2$

$V_1 = I_1 R_1$
 $7.2 = I_1 \cdot 6$
 $\frac{7.2}{6} = I_1$
 $1.2A = I_1$

$V_2 = I_2 R_2$
 $7.2 = I_2 \cdot 4$
 $\frac{7.2}{4} = I_2$
 $1.8A = I_2$