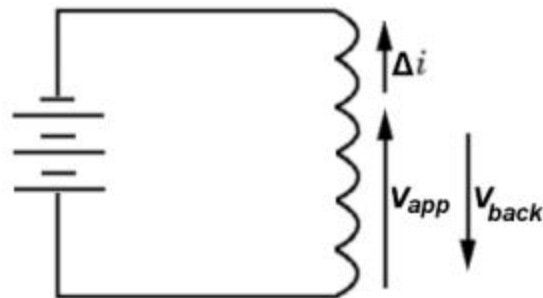


# Transformers

more than meets the eye...

When you turn on a circuit with just a resistor in it the current reaches its steady state almost instantly.

This is not true when we have a coil in a circuit (Inductor - L).




Changing current and back EMF in a coil\*

$$V_{net} = V_{applied} - V_{back}$$

This is because the current that you send through the wire creates a  $\vec{B}$  of its own. This opposes the current in the wire and has the wire 'fight' that field. As long as the current is changing the  $\vec{B}$  will work against it. Eventually there comes an equilibrium and the inductor works as a short circuit.

Once the circuit is turned off, the opposite is true. The current will decrease (this is a change in  $\vec{B}$ ) and the  $\vec{B}$  will oppose the lack of current and it will continue for a time afterwards.

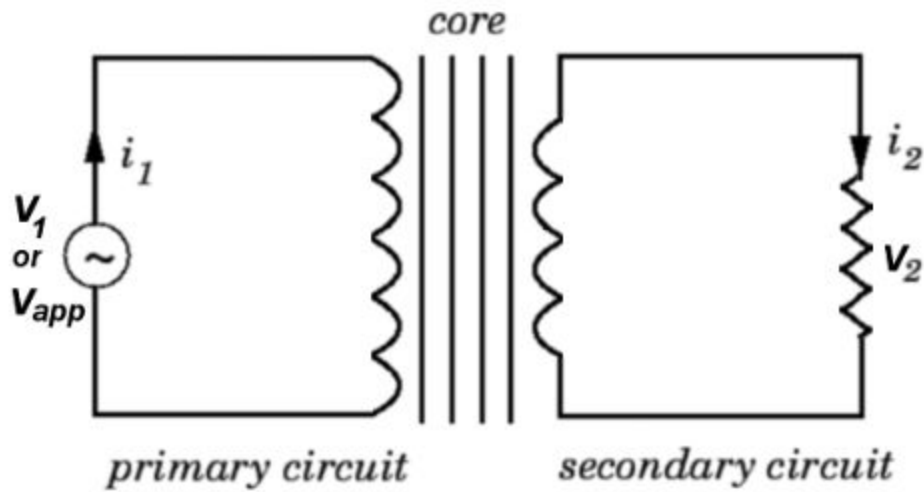The above picture is  $\frac{1}{2}$  a transformer. We take this concept and double it...



Closed 2ndary circuit


In this case we send a current through the left circuit and it creates a  $\vec{B}$ . This has an effect on the secondary circuit and creates a current there. Wireless electricity! I've seen this done in a lab and we got a light bulb to light a meter away without connection to anything. Pretty sweet.

Now, we use this concept to build our transformer.



The primary coil has more turns than the secondary coil. This is called a step down transformer. The voltage in the secondary coil is lower than that of the primary.

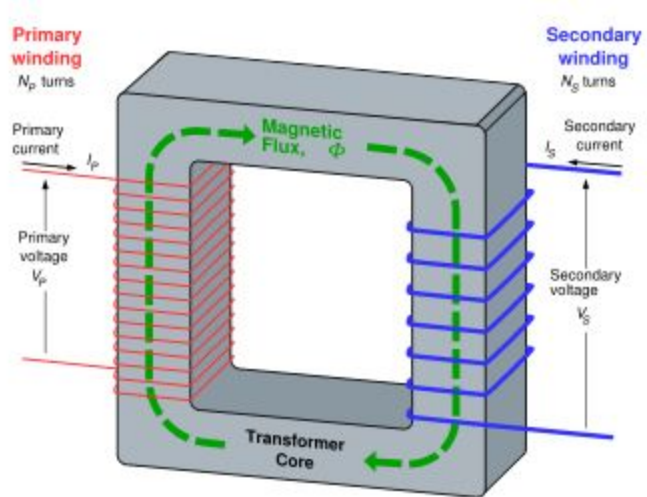A step up transformer simply has the coils in the opposite orientation.



Let's build the equation:

$\varepsilon_p = -N_p \frac{\Delta\Phi_p}{\Delta t}$  also,  $\varepsilon_s = -N_s \frac{\Delta\Phi_s}{\Delta t}$ . We are interested in the ratio of voltage in the primary and the secondary so we need to divide  $\frac{\varepsilon_p}{\varepsilon_s}$ . This gives us our step up / down equation:

$$\frac{\varepsilon_p}{\varepsilon_s} = \frac{N_s}{N_p} = \text{constant} = k$$

The astute among you may have wondered how we get this  $\Delta V$  for nothing. The law of conservation of energy still applies. Input still must equal output. The tradeoff is in current.

$$\begin{aligned} P_p &= P_s \\ I_p V_p &= I_s V_s \\ \therefore \frac{V_p}{V_s} &= \frac{I_s}{I_p} \end{aligned}$$

Transformers are used to

- a) Increase AC
- b) Decrease AC
- c) Both A & B
- d) Keep AC constant

Transformers are an application of

- a) Induction
- b) Mutual induction
- c) Electrostatics
- d) Mutual Charges

If the secondary voltage is higher than the primary voltage the transformer is called a

- a) Step up transformer
- b) Step down transformer
- c) Inductor
- d) Resistor

An ideal transformer dissipates

- a) Unit power
- b) Infinite power
- c) Zero Power
- d) Limited Power

If an AC source is 240V and a transformer supplies 12V to a model train which draws current of .8A, then the primary current is

- a) .4A
- b) .04A
- c) 1A
- d) 2A

Hint: C B A C B