

# C-C-C-C-Combo!


Let's put it all together.
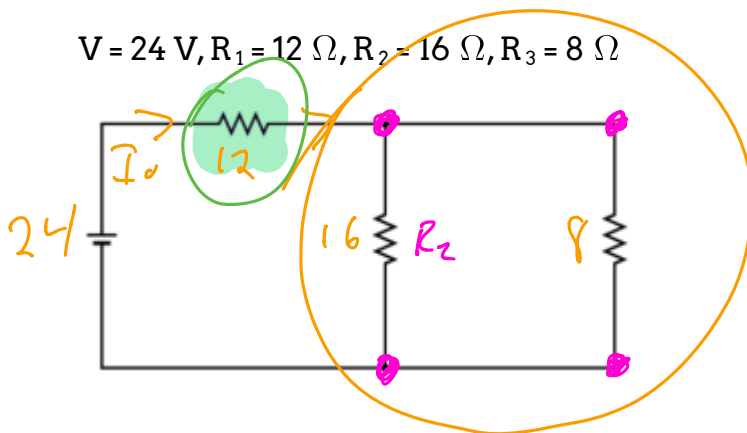
## Series + Parallel = Most\_Awesome\_Circuits

- Combination circuits have sections that are in series and sections that are in parallel
- To solve these we will simplify them until we have the simplest version of the circuit and then find the fundamental properties
- We start with sections furthest from the battery and simplify working towards the battery



$$V = 24 \text{ V}, R_1 = 12 \ \Omega, R_2 = 16 \ \Omega, R_3 = 8 \ \Omega$$



$$\begin{aligned} V_1 &= I_1 R_1 \\ &= 1.38(12) \\ &= 16.6 \text{ V} \end{aligned}$$

$$\begin{aligned} V_2, V_3 &= 24 - 16.6 \\ &= 7.4 \text{ V} \end{aligned}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\begin{aligned} \frac{1}{R_p} &= \frac{1}{16} + \frac{1}{8} \\ &= \frac{3}{16} \end{aligned}$$

$$R_p = \frac{16}{3} = 5.33 \ \Omega$$

$$\begin{array}{l|l} V_2 = I_2 R_2 & V_3 = I_3 R_3 \\ 7.4 = I_2 16 & 7.4 = I_3 8 \\ \frac{7.4}{16} = I_2 & \frac{7.4}{8} = I_3 \\ 0.46 = I_2 & 0.92 = I_3 \end{array}$$



We're missing too much information to move forward.  
Let's see if combining the parallel resistors will help:



$$V = I_o R$$
$$24 = I_o 17.33$$
$$\frac{24}{17.33} = I_o$$
$$1.38 A = I_o$$


$$V = IR \quad V = 2.24(10)$$

$$V = 22.4$$

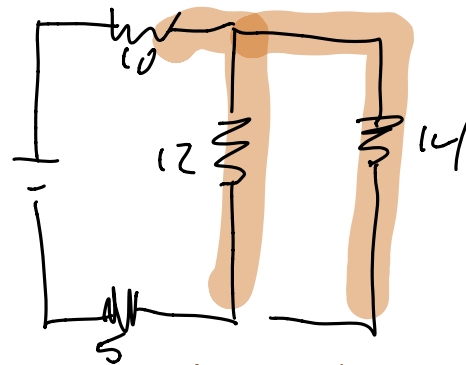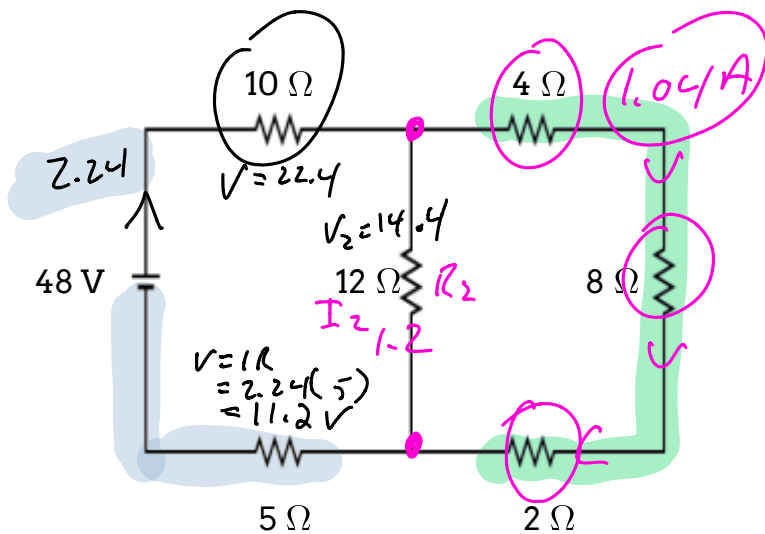


$$\frac{1}{R_p} = \frac{1}{12} + \frac{1}{14}$$

$$R_p = 6.46 \Omega$$

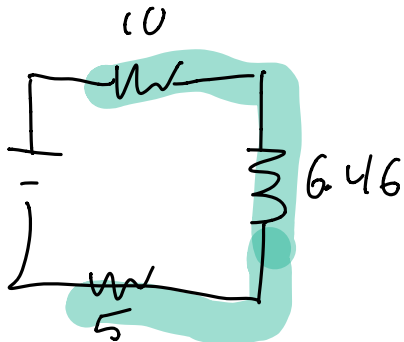

$$R_T = 10 + 6.46 + 5$$

$$= 21.46 \Omega$$

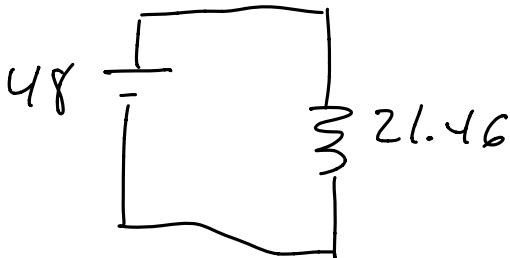


$$V = IR$$

$$48 = I \cdot 21.46$$





$$\frac{48}{21.46} = I$$

$$2.24 A = I_0$$

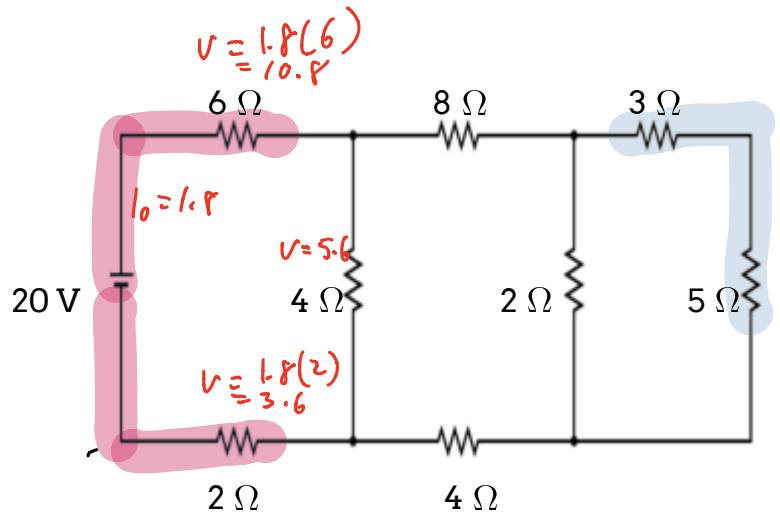


$$\frac{1}{R_p} = \frac{1}{2} + \frac{1}{8}$$

$$R_p = 1.6 \Omega$$

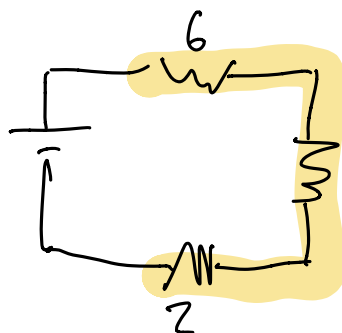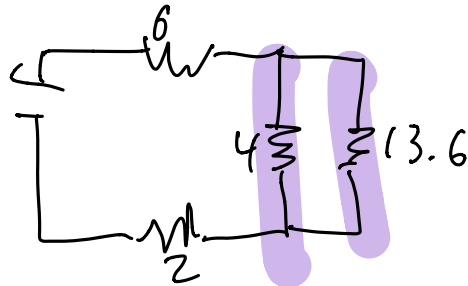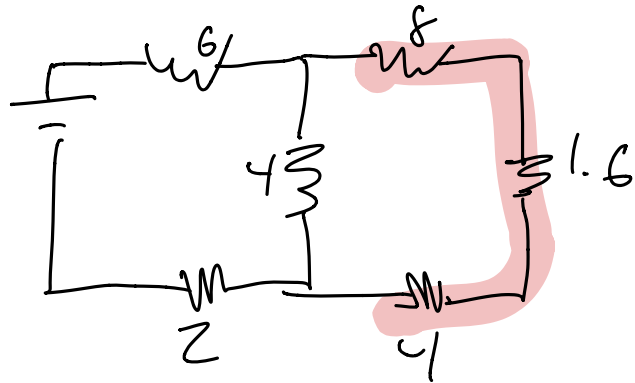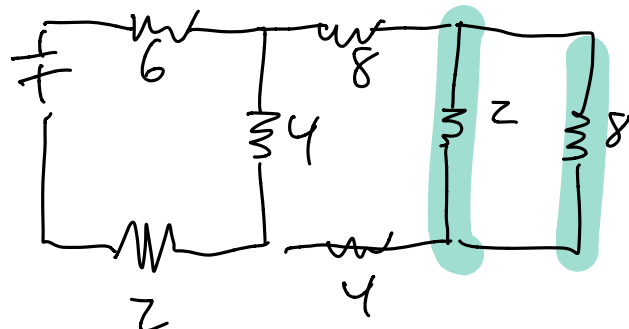

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{13.6}$$

$$R_p = 3.09 \Omega$$

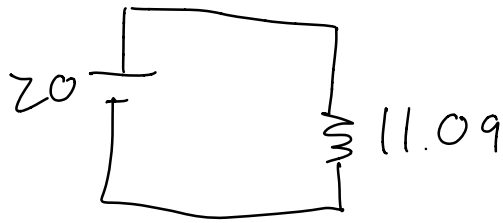

$$V = IR$$

$$\frac{20}{11.09} = I$$

$$1.8A = I$$