
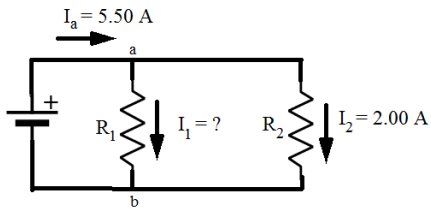


6.2 Kirchoff's Laws


1. Determine I_1

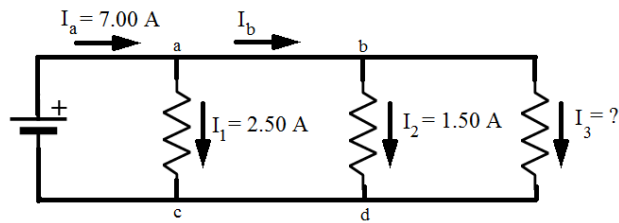


2. Determine I_b, I_3




3. Determine I_x

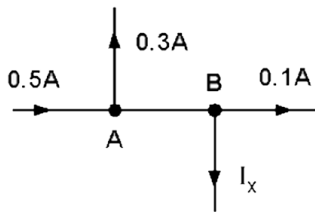


4. Determine I_1

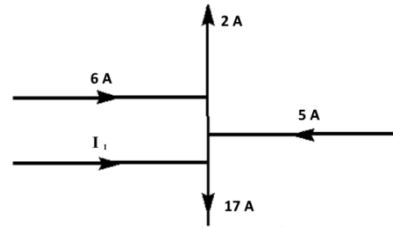


5. Determine I_1, I_2, I_3, I_4, I_5

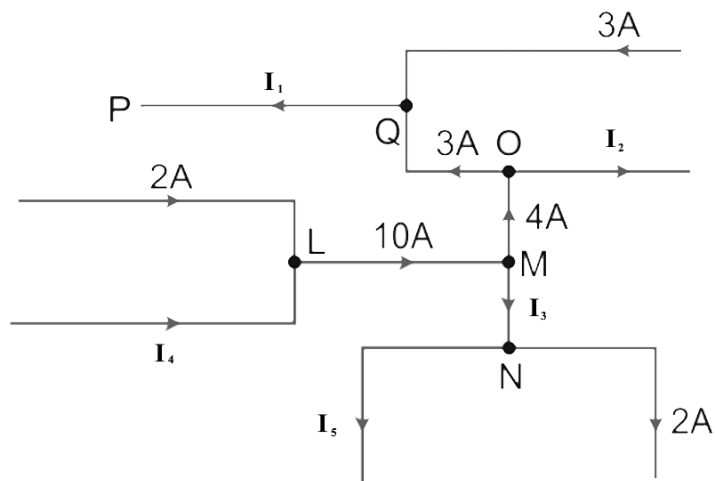


6. Determine V

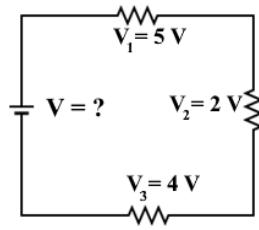

7. Determine V_1, V_2

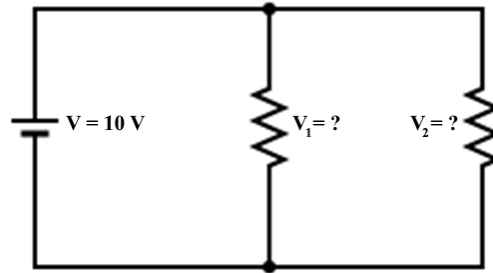

8. Determine V, V_1, V_2

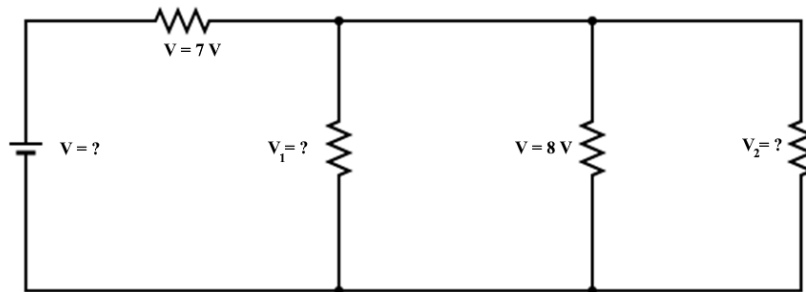

9. Determine V_1, V_2, V_3

