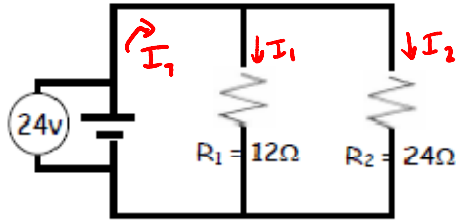


### 6.4 Parallel Circuits


1.



$$R_p = R_{eq} = \underline{8\ \Omega} \quad I_T = \underline{3\ A} \quad V_1 = \underline{24\ V}$$

$$V_2 = \underline{24\ V} \quad I_1 = \underline{2\ A} \quad I_2 = \underline{1\ A}$$

2.

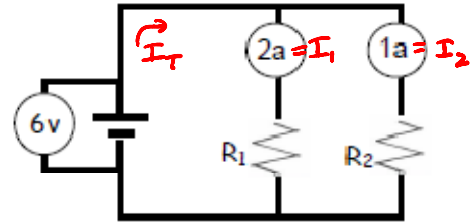


$$V_1 = \underline{6\ V} \quad V_2 = \underline{6\ V}$$

$$R_1 = \underline{3\ \Omega} \quad R_2 = \underline{6\ \Omega} \quad R_{eq} = \underline{2\ \Omega}$$

$$I_1 = \underline{2\ A} \quad I_2 = \underline{1\ A} \quad I_T = \underline{3\ A}$$

3.

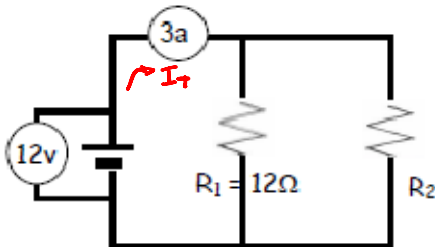


$$V_1 = \underline{12\ V} \quad V_2 = \underline{12\ V}$$

$$I_T = \underline{3\ A} \quad I_1 = \underline{1\ A} \quad I_2 = \underline{2\ A}$$

$$R_2 = \underline{6\ \Omega} \quad R_{eq} = \underline{2\ \Omega}$$


4.

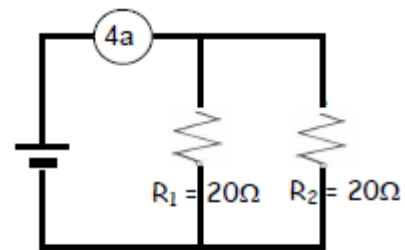

$$R_{eq} = \underline{10\ \Omega} \quad I_T = \underline{4\ A} \quad V_T = \underline{40\ V}$$

$$V_1 = \underline{40\ V} \quad I_1 = \underline{2\ A} \quad I_2 = \underline{2\ A}$$

5.

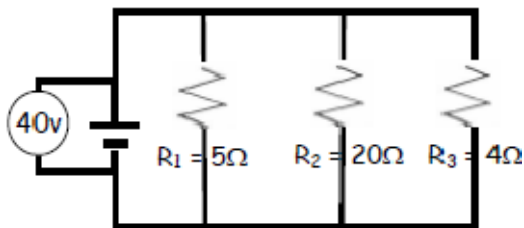


$$R_{eq} = \underline{2\ \Omega} \quad I_T = \underline{20\ A}$$

$$V_1 = \underline{40\ V} \quad V_2 = \underline{40\ V} \quad V_3 = \underline{40\ V}$$

$$I_1 = \underline{8\ A} \quad I_2 = \underline{2\ A} \quad I_3 = \underline{10\ A}$$

6.

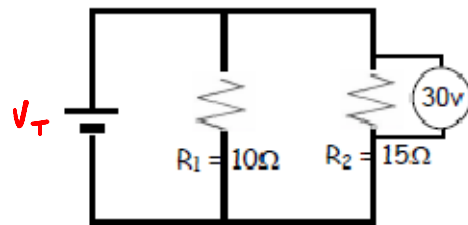

$$V_1 = \underline{30\ V} \quad V_T = \underline{30\ V}$$

$$I_1 = \underline{3\ A} \quad I_2 = \underline{2\ A}$$

$$R_{eq} = \underline{6\ \Omega} \quad I_T = \underline{5\ A}$$