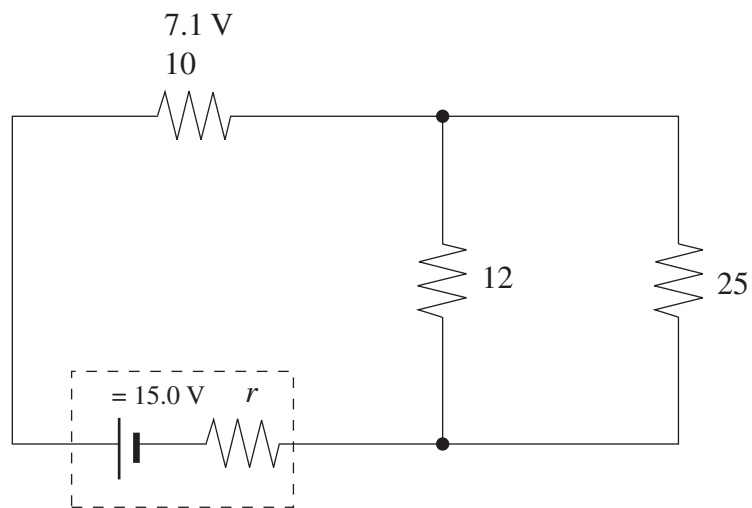


1. The potential difference across the 10 Ω resistor is 7.1 V.



- a) What is the power dissipated by the $25\ \Omega$ resistor?


(4 marks)

- b) What is the internal resistance of the battery?


(3 marks)

2. a) For the circuit below, what is the terminal voltage of the battery?

(4 marks)

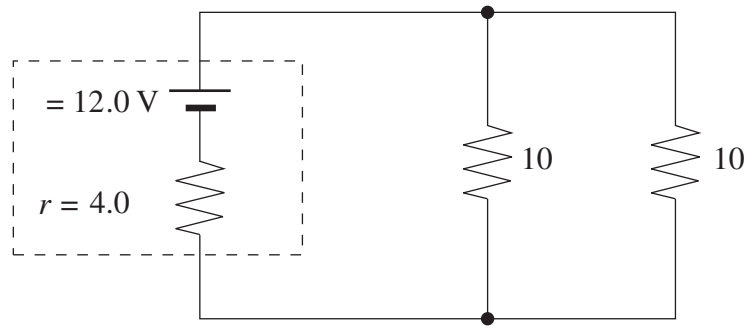

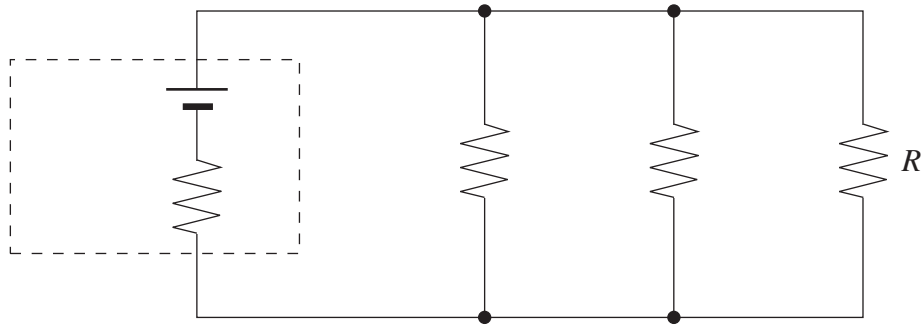
- b) If resistor R is added in parallel to the circuit as shown, what is the effect on the terminal voltage? (1 mark)



- increase
- no change
- decrease

- c) Using principles of physics, explain your choice for b). (4 marks)

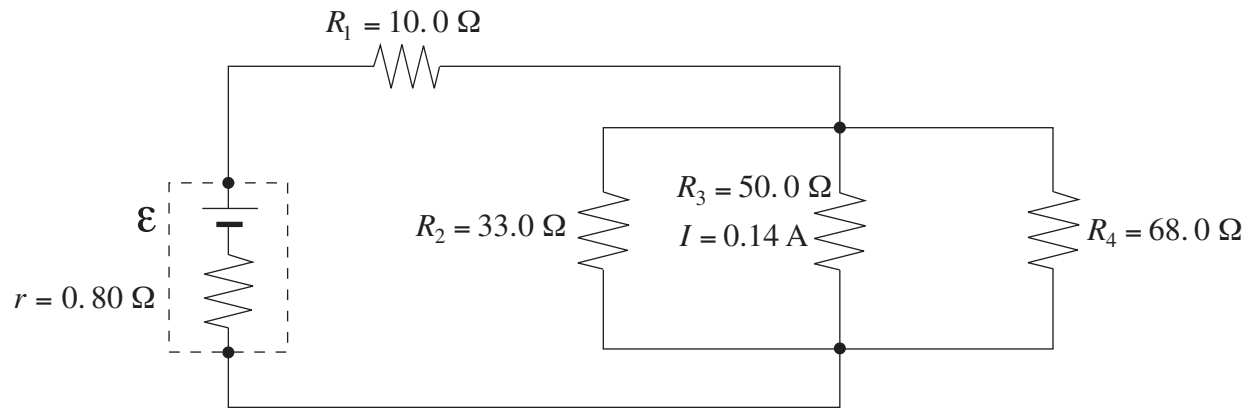3. The current through the 50.0Ω resistor in the circuit below is 0.14 A .




a) Determine the emf of the battery.

(5 marks)

b) Determine the power dissipated in the battery's internal resistance.

(2 marks)

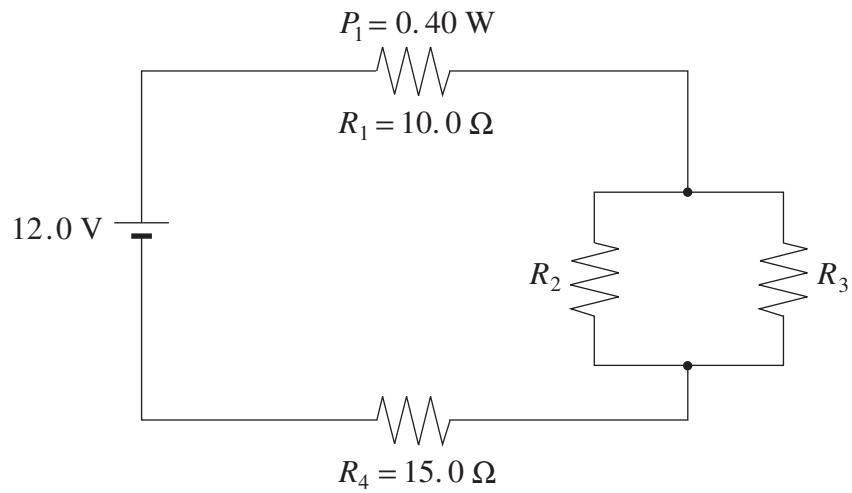4. In the circuit below, resistor R_1 dissipates 0.40 W . Resistors R_2 and R_3 are identical.



What is the resistance of R_2 ?

(7 marks)

5. A 12 V battery from a car is used to operate a 65 W headlight.

a) How much energy does the headlight use in 1.5 hours?

(2 marks)

b) What total charge passes through the headlight during this time?

(3 marks)

c) What is the total number of electrons that pass through the headlight during this time period?

(2 marks)

6. A 12 V battery transfers 33 C of charge to an external circuit in 7.5 s.

a) What current flows through the circuit?

(2 marks)

b) What is the resistance of the circuit?

(2 marks)

c) What is the power output of the battery?

(2 marks)

d) The external circuit is most likely to consist of

a bulb.


a kettle.

a calculator.


(Check one response.)

(1 mark)

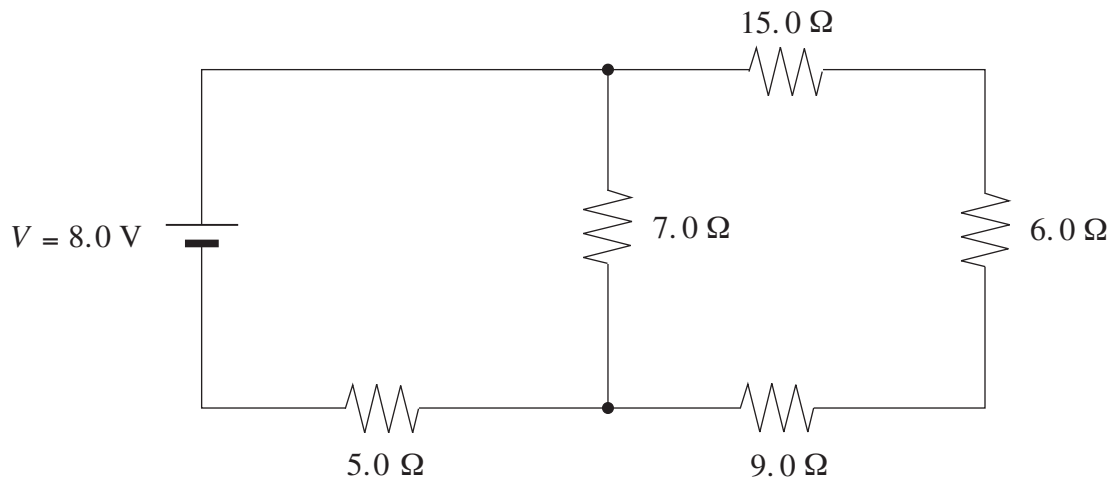7. What is the potential difference across the 6.0Ω resistor in the circuit shown? (7 marks)




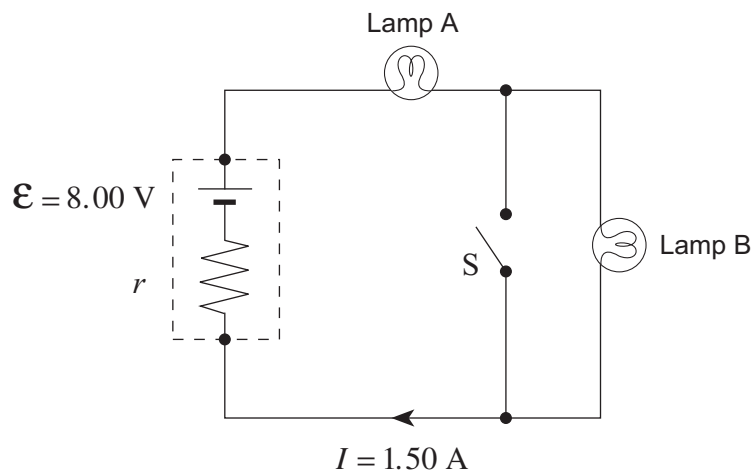8. The circuit shown consists of an 8.00 V battery and two light bulbs. Each light bulb dissipates 5.0 W. Assume that the light bulbs have a constant resistance. Switch S is open.



- a) If a current of 1.50 A flows in the circuit, what is the internal resistance r of the battery?
(4 marks)

b) The switch S is now closed.

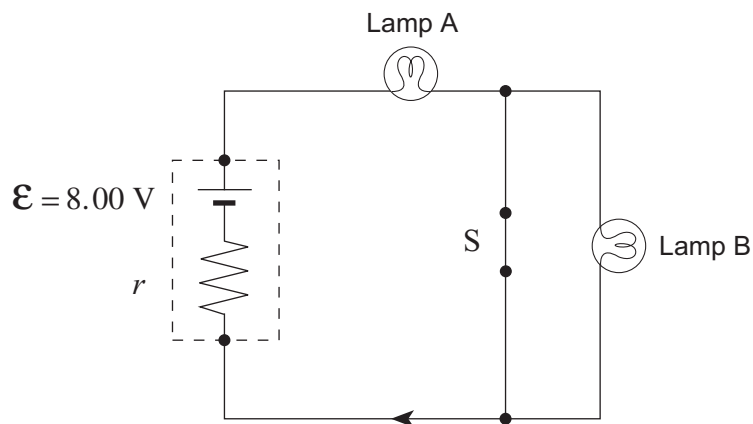

Lamp A will now be

- i) brighter.
- the same brightness as before.
- dimmer.

(Check one response.)

(1 mark)

The battery's terminal voltage will now be

- ii) greater than before.
- the same as before.
- less than before.


(Check one response.)

(1 mark)

c) Using principles of physics, explain your answers to b).

(3 marks)

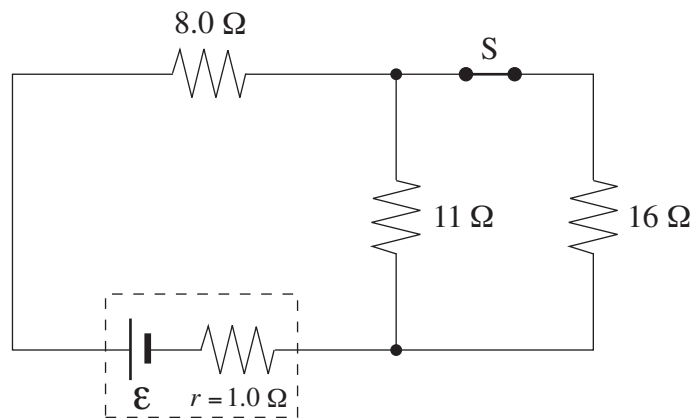9. The terminal voltage of the battery is 5.8 V.



a) What is the emf of this battery?


(6 marks)

b) What is the effect on the emf of the battery when switch S is opened?


(1 mark)

10. How much energy does the $6.0\ \Omega$ resistor dissipate in 15 seconds in the circuit shown?

(7 marks)

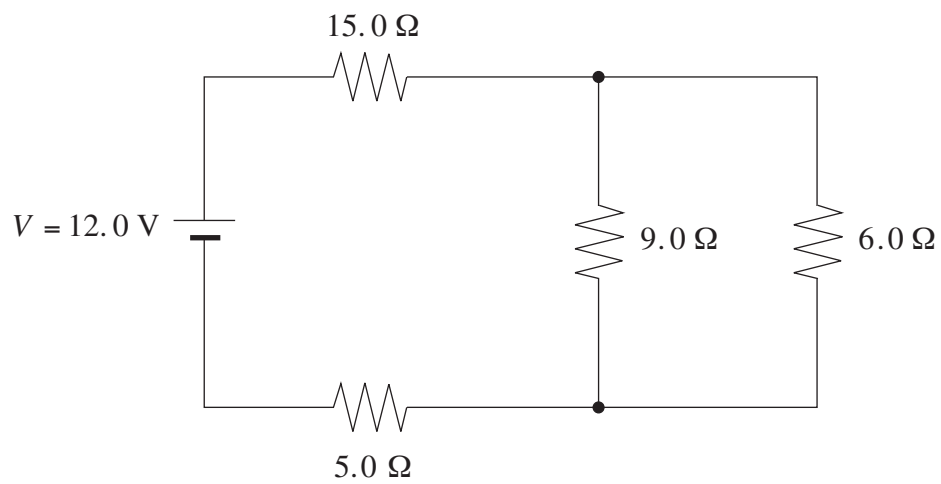

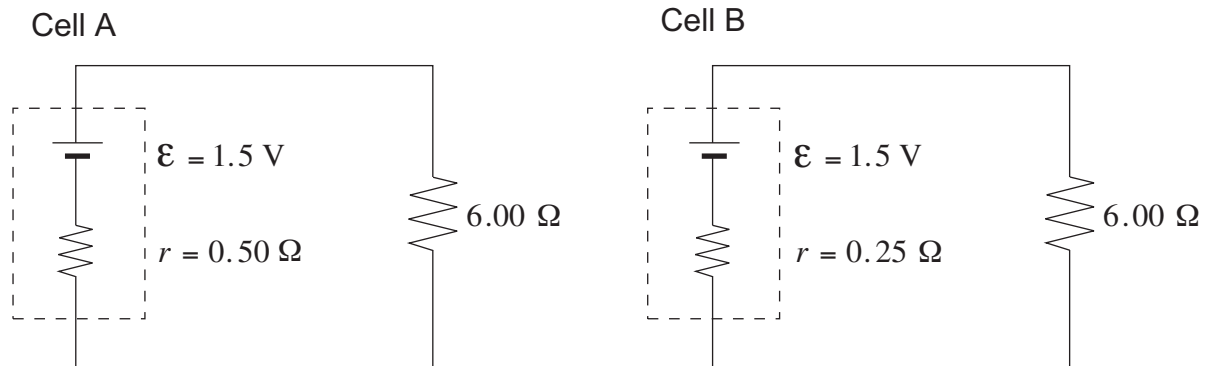11. Each of the two cells shown is connected to an external 6.00Ω resistor.



With supporting calculations, state which cell delivers the greater power to the 6.00Ω resistor.
(7 marks)