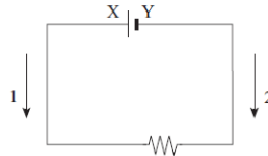


## Unit 6 Review

1. A 9.0 V battery was recharged with a current of 1.2 A in  $1.8 \times 10^4$  s. How much charge was transferred during that time?

2. Which of the following correctly labels arrows 1 and 2 and polarities X and Y in the circuit below.




	ARROW 1	ARROW 2	POLARITY X	POLARITY Y
A.	Electron Flow	Conventional Current	Positive	Negative
B.	Electron Flow	Conventional Current	Negative	Positive
C.	Conventional Current	Electron Flow	Positive	Negative
D.	Conventional Current	Electron Flow	Negative	Positive

3. Current is a measure of


- A. the number of charges stored in a cell.
- B. the amount of energy given to a charged object.
- C. the charge passing a point in a circuit in a given time.
- D. the resistance to the flow of charged particles in a circuit.

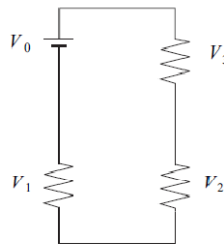4. Which of the following relationships correctly applies to the circuit shown below?



- A.  $V_0 = V_1 + V_2 + V_3$
- B.  $V_0 + V_1 = V_2 + V_3$
- C.  $V_0 = V_1 = V_2 = V_3$

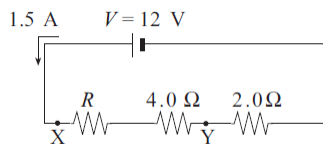
5. In the following circuit, what is the magnitude of the potential difference between X and Y?




6. A potential difference of 12 V causes 0.35 C of electric charge to pass through a resistor in 2.6 s. What power does the resistor dissipate?
7. The headlights in a car use 95 W of power. A driver parks her car but leaves the lights on. The 12 V battery has  $3.4 \times 10^5$  C of stored charge. How long does it take for the battery to lose its charge?
8. Which of the following household electrical appliances has the greatest rate of energy consumption?

	ITEM	VOLTAGE	CURRENT
A.	Video Camera	6.0 V	1.6 A
B.	Radio	4.5 V	0.45 A
C.	Cassette Recorder	6.0 V	2.2 A
D.	Ghetto Blaster	12 V	1.4 A

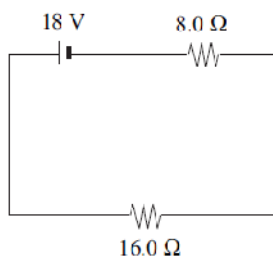9. Calculate the power dissipated by the  $8.0\ \Omega$  resistor in the circuit below.



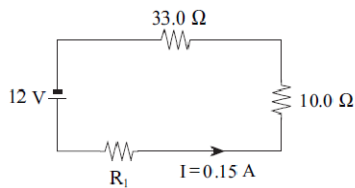10. What is the power dissipated in resistor  $R_1$  in the circuit shown in the diagram below?




11. A battery whose emf is 6.0 V is connected to a 2.0 Ω resistor. The voltage drop across the 2.0 Ω resistor is 5.0 V. What is its internal resistance?


12. The terminal voltage of a battery is always less than the emf of a battery when supplying current in a circuit because of a voltage drop due to

- A. the terminal connections.
- B. the battery's internal resistance.
- C. heating of resistors in the circuit.
- D. heating of the wires in the circuit.

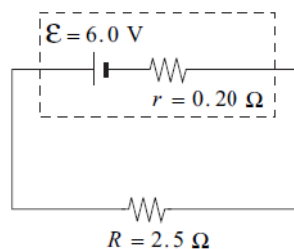13. What is the terminal voltage of the battery in the circuit shown in the diagram?




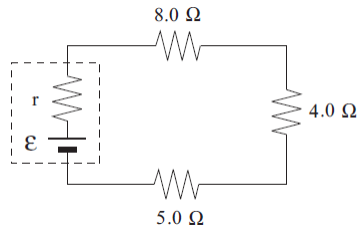14. When a resistor is added in parallel with the  $4.0\ \Omega$  resistor in the circuit shown below, what happens to the voltage across the  $5.0\ \Omega$  resistor and to the terminal voltage of the battery?




	VOLTAGE ACROSS $5.0\ \Omega$	TERMINAL VOLTAGE
A.	increases	decreases
B.	increases	increases
C.	decreases	decreases
D.	decreases	increases

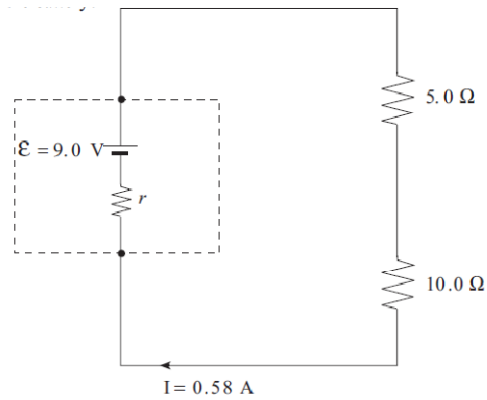
15. In the following circuit, what is the power loss in the battery?



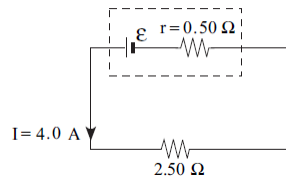
16. What is the emf of the battery shown?



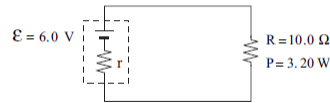17. A battery provides 3.20 W of power to an external resistance. What power is dissipated as heat by the internal resistance within the battery?



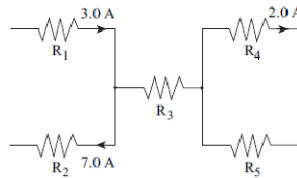18. The diagram below shows part of an electrical circuit.




What are the magnitude and direction of the current passing through resistor R5 ?

19. What happens to the total resistance of a circuit as one more resistor is added in parallel?


- A. The total resistance decreases.
- B. The total resistance increases.
- C. The total resistance becomes zero.
- D. The total resistance does not change.

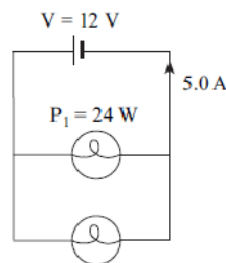20. A 12 V battery supplies a 5.0 A current to two light bulbs as shown below.




The power output of one of the bulbs is  $P_1 = 24 \text{ W}$ . What is the power output of the other bulb?

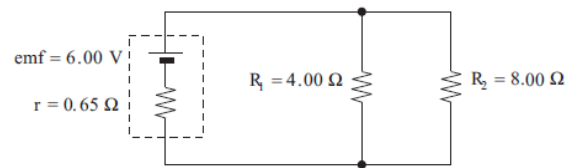
21. What current flows through the  $4.00\ \Omega$  resistor in the following circuit?





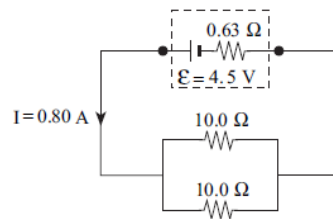
22. What is the terminal voltage of the cell in the circuit shown in the diagram below?



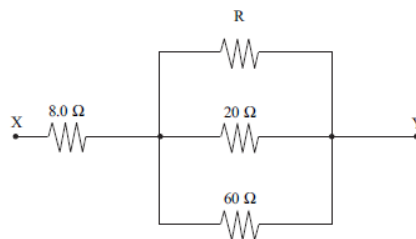
23. The total resistance between points X and Y is  $14.0\ \Omega$ . What is the value of R?



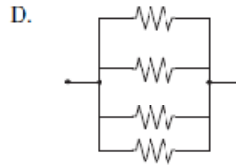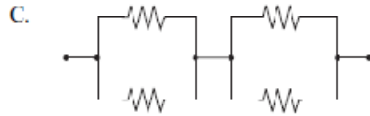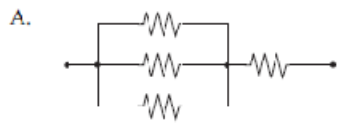25. Which of the following arrangements would draw the smallest current when connected to a potential difference? All resistors have the same value.




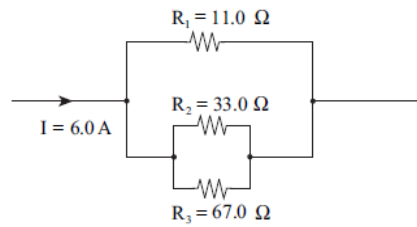26. The diagram below shows part of an electrical circuit.




What is the current through resistor  $R_1$ ?

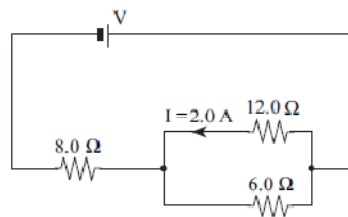
27. What is the voltage,  $V$ , of the power supply shown in the circuit?



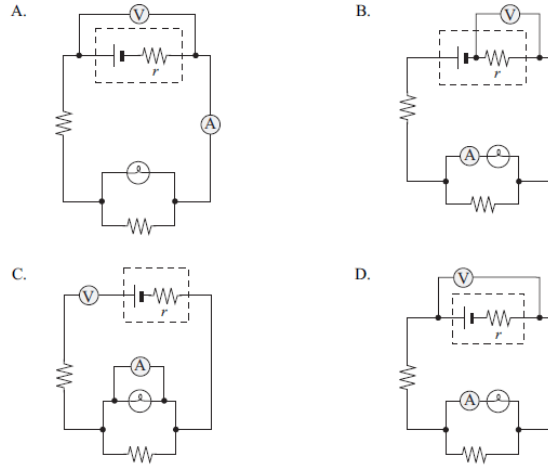
28. In which of the following circuits is the voltmeter placed correctly to measure the terminal voltage of the battery, and the ammeter placed correctly to measure the current through the light bulb?



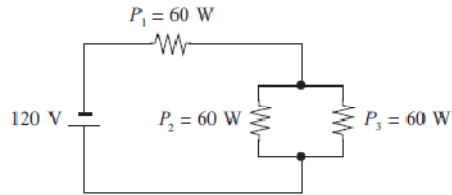29. What is the current leaving the battery in the circuit below?




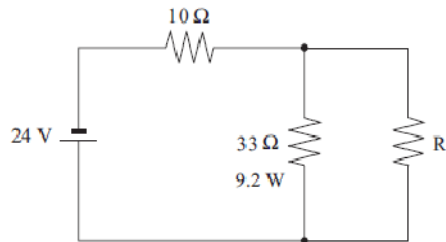30. What is the total power dissipated by the three resistors in the circuit shown below?






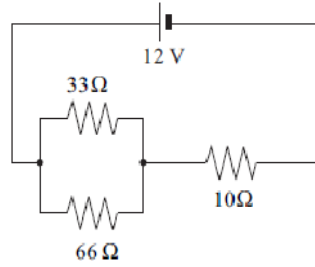31. What is the current through the 10 resistor in the circuit shown below?




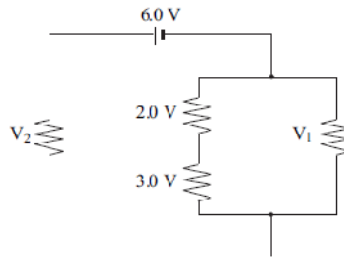32. What are the potential differences,  $V_1$  and  $V_2$ , in the circuit shown below?



	Potential Difference $V_1$	Potential Difference $V_2$
A.	1.0 V	5.0 V
B.	1.0 V	6.0 V
C.	5.0 V	1.0 V
D.	5.0 V	5.0 V

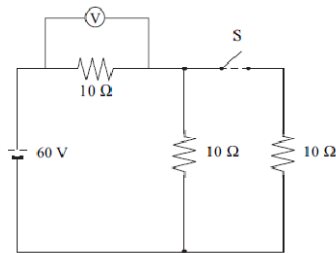
33. In the circuit shown below, voltmeter readings are taken when switch is closed and open.



Which of the following is correct?

VOLTMETER READINGS	
SWITCH CLOSED	SWITCH OPEN
A.	20 V      30 V
B.	30 V      30 V
C.	40 V      20 V
D.	40 V      30 V

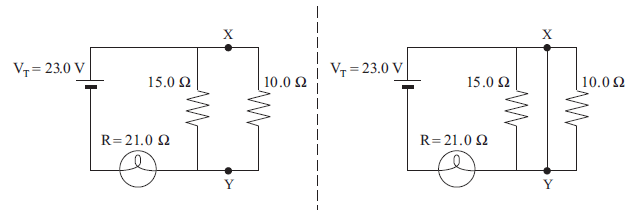
34. A circuit is made from two resistors and a light bulb as shown on the left. A short time later a copper wire is connected across points X and Y as shown on the right diagram.




What is the current through the light bulb and what happens to the brightness of the bulb when the wire is connected?

	CURRENT	BRIGHTNESS OF BULB
A.	0.64 A	dimmer
B.	0.64 A	brighter
C.	1.10 A	dimmer
D.	1.10 A	brighter

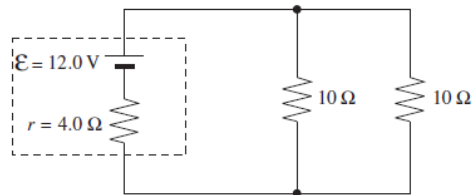35. a) For the circuit below, what is the terminal voltage of the battery?




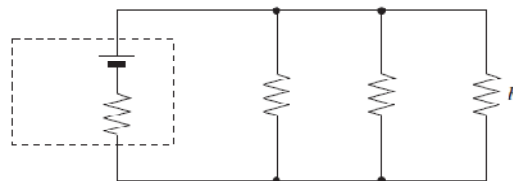b) If resistor  $R$  is added in parallel to the circuit as shown, what is the effect on the terminal voltage?




- increase
- no change
- decrease

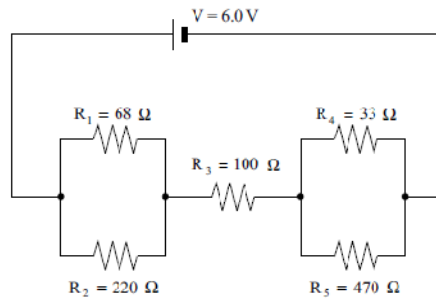36. Consider the circuit shown in the diagram below.




- What is the total resistance of the circuit?
- What is the current through the  $100 \Omega$  resistor?
- What is the power dissipated in the  $100 \Omega$  resistor?

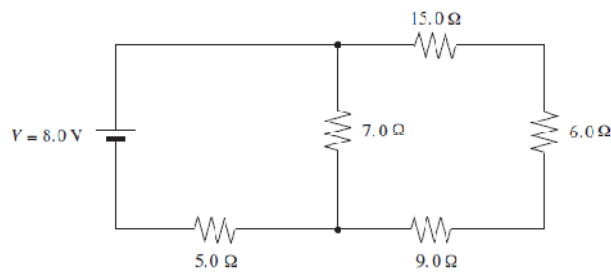37. What is the potential difference across the  $6.0 \Omega$  resistor in the circuit shown?




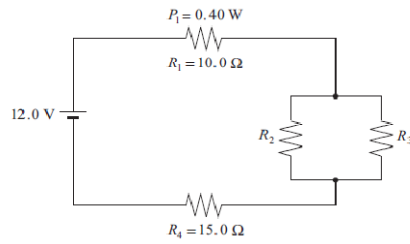38. In the circuit below, resistor  $R_1$  dissipates 0.40 W. Resistors  $R_2$  and  $R_3$  are identical.



What is the resistance of  $R_2$ ?

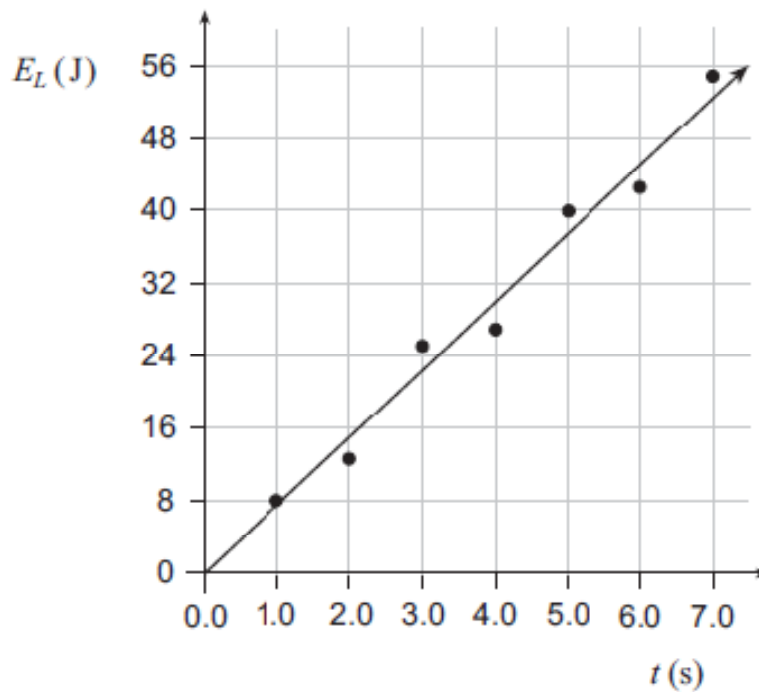39. The graph shows the light energy  $E_L$  emitted by a bulb versus time  $t$ .



Find the power output of the bulb.


40. A 12 V battery from a car is used to operate a 65 W headlight.

a) How much energy does the headlight use in 1.5 hours?

b) What total charge passes through the headlight during this time?

c) What is the total number of electrons that pass through the headlight during this time period?

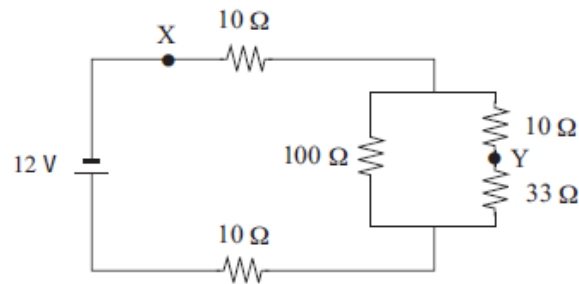41. What is the potential difference between points X and Y?



Answers: 1)  $2.2 \times 10^4$  2) C 3) C 4) A 5) 9 V 6) 1.62 W 7) 42900 s 8) D 9) 4.5 W 10) 0.83W  
11) 0.4 Ω 12) B 13) 5.6 V 14) A 15) 0.17 W 16) 12 V 17) 0.19 W 18. 6 A left 19) A  
20) 36 W 21) 1.2 A 22) 4.0 V 23) 10 Ω 24. A 25) 4 A 26) 72 V 27) D 28) 1.5 A  
29) 16 W 30) 0.37 A 31) C 32) D 33. D 34a) 6.7 V 34b) decrease 35a) 182.7 Ω  
35b)  $3.3 \times 10^{-2}$  35c) 0.11 W 36) 0.85 V 37) 70 Ω 38) 7.6 W 39a)  $3.5 \times 10^5$  J 39b) 29000 C  
39c)  $1.8 \times 10^{23}$  40) 4.07 V